

Sequential Circuit: Flip Flops


Sequential Circuit



A Sequential circuit is a combinational circuit with memory or storage element in feedback i.e Sequential circuit' output depends on inputs as well as previous state of storage element.

Synchronous Sequential Circuit: Behaviour of the system depends on inputs (external and internal state) only at discrete instants of time. Storage elements used are clocked Flip Flops

 Asynchronous Sequential Circuit: Behaviour of the system depends on inputs (external and internal state) at any time. Storage element used are time delay elements and latches




Sequential Circuit

Latch



- Latch holds 1 bit of information
- Two outputs are complementary
- Inputs are S and R which Sets (output 1) and Resets (output 0) the latch
- $S=R=1$ is invalid in which rule of complementary output breaks

Characteristics table of SR Latch				Full State table of SR Latch			
S	R	Q_{n+1}		S	R	Q_n	Q_{n+1}
0	0	Q_n	No Change	0	0	0	0
0	0			0	0	1	1
0	1	0	Reset	0	1	0	0
0	1			0	1	1	0
1	0	1	Set	1	0	0	1
1	0			1	0	1	1
1	1	Invalid		1	1	0	invalid
				1	1	1	invalid

 

SR Latch using NOR gate

SR Flip Flop





- In Latch, spurious inputs can cause output change at time.
- A clock pulse (in AND to inputs) ensures that inputs are applied only when clock pulse is present

Characteristics table of SR FF				Full State table of SR FF			
S	R	Q_{n+1}		S	R	Q_n	Q_{n+1}
0	0	Q_n	No Change	0	0	0	0
0	1	0	Reset	0	0	1	1
1	0	1	Set	0	1	0	0
1	1	Invalid		0	1	1	0
				1	0	0	1
				1	0	1	1
				1	1	0	invalid
				1	1	1	invalid

$$Q_{n+1}(J, K, Q_n) = \sum (1, 4, 5) + \phi(6, 7)$$

  SR Characteristics equation $Q_{n+1} = S\bar{Q} + \bar{R}Q_n$; and $SR \neq 1$



JK Flip Flop





- JK is modification of SR FF for invalid input combination
- For J=K=1, output Toggles (complements)

Characteristics table of JK FF				Full State table of JK FF			
J	K	Q_{n+1}		J	K	Q_n	Q_{n+1}
0	0	Q_n	No Change	0	0	0	0
0	1	0	Reset	0	0	1	1
1	0	1	Set	0	1	0	0
1	1	$\overline{Q_n}$	Toggle	0	1	1	0
				1	0	0	1
				1	0	1	1
				1	1	0	1
				1	1	1	0

$$Q_{n+1}(J, K, Q_n) = \sum (1, 4, 5, 6)$$
  
$$\text{JK Characteristics equation } Q_{n+1} = J\overline{Q_n} + \overline{K}Q_n$$





JK Flip Flop symbol

T Flip Flop



- T FF is JK FF with J=K
- For T=1, output Toggles (complements)

Characteristics table of T FF			Full State table of T FF		
T	Q_{n+1}		T	Q_n	Q_{n+1}
0	Q_n	No Change	0	0	0
			0	1	1
1	$\overline{Q_n}$	Toggle	1	0	1
			1	1	0

  

T Characteristics equation

$$Q_{n+1}(T, Q_n) = \sum (1, 2)$$

$$Q_{n+1} = T\overline{Q_n} + \overline{T}Q_n = T \oplus Q_n$$

T Flip Flop symbol

D Flip Flop





- D FF is JK FF with $J=D$ and applying NOT gate between J and K
- Output is same as Data input (D)

Characteristics table of D FF			Full State table of T FF		
D	Q_{n+1}		D	Q_n	Q_{n+1}
0	0	Reset	0	0	0
0	0		0	1	0
1	1	Set	1	0	1
1	1		1	1	1

$$Q_{n+1}(D, Q_n) = \sum(2,3)$$

D Characteristics equation

$$Q_{n+1} = D$$

 
 


D Flip Flop symbol

JK Flip Flop: Race around condition



  - when $J=K=1$, output toggles recursively during active period of clock pulse
- This leads to unpredictable output state after active period of clock pulse
- This condition is known as race around condition




- Solution to race around condition
 - Master slave FF: that gives a single trigger at slave output. However race around condition occurs in Master.
 - **Edge triggered FF**: flip-flop triggers the 'edge' of clock pulse


Edge Triggered Flip Flop



 
- Edge triggered FF considers input values at the edge of the clock pulse (either positive or negative)



 - Timing diagram of typical positive edge triggered JK FF



Positive Edge triggered JK FF


 


Negative Edge triggered JK FF

Edge Trigger Circuit



  - Edge triggered FF considers input values at the edge of the clock pulse (either positive or negative)



Positive edge pulse train generation circuit

- Circuit generates a pulse train of pulse duration equal to delay time of invert gate (comparable to rise time or edge duration of clock pulse)
- Narrow pulse duration allows only one input trigger in clock pulse

Conversion of Flip-flops



T → JK FF conversion


- Requires design of additional combination circuit (as shown in figure)

Step 1: Write the desired state table (JK State table)

Step 2: Determine what should be value at available FF input for desired state changes (what should be at T to cause $Q_n \rightarrow Q_{n+1}$ using excitation table of T

Step 3: Write output of additional circuit (T) in SOP and minimize using K map

Step 4: Implement the function

 

Conversion of Flip-flops




T → JK FF conversion

J	K	Q_n	Q_{n+1}	T
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	1

$$T(J, K, Q_n) = \sum (3, 4, 6, 7)$$

Solving using K map

$$T = J\overline{Q_n} + KQ$$

 

T FF to JK FF Conversion

T FF excitation table		
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0