

READ ONLY MEMORY

(ROM)

SYED HASAN SAEED

hasansaeedcontrol@gmail.com

<https://shasansaeed.yolasite.com>

ROM

- In ROM Binary information is stored permanently.
- Block diagram of ROM (size $m \times n$) is shown in fig.1, where 'm' is the number of locations and 'n' is the number of bit words that can be stored in each location.

 


Fig. 1

 


Fig. 2

ROM

- There are 'k' number of address lines to access 'm' locations.
$$m = 2^k$$
- 'n' is the data output lines. This gives the data bits of the stored word selected by the address.
- Therefore for implementation of 'k' variables and 'n' outputs then the size of ROM is represented by $2^k \times n$ as shown in fig.2. this will generate all possible 2^k minterms.
- ROMs are designed only for reading the stored information.
- ROM does not have write operation i.e. user cannot write any information.
- ROM is used to store fixed information like instructions, look up tables etc.

ROM

- ROMs are programmed at the time of manufacturing.
- ROMs are costly.
- ROMs can be used for the implementation of combinational circuits

EXAMPLE 1

The following memory units are specified by the number of words times the number of bit per word. How many address lines and input-output data lines are required in each case.

(i) 4K x 16 (ii) 2G x 8 (iii) 16M x 32 (iv) 256K x 64

Reference: Moris Mano

Solution: (i) since, $1K=1024=2^{10}$

$$4K=2^2 \times 2^{10}=2^{12}$$

4K x 16 can be written as $2^{12} \times 16$

Therefore, there are 12 address lines and 16 data lines.

Total input-output lines = $12+16=32$

(ii) 2G x 8

$$1\text{ G} = 2^{30}$$

$$2\text{G} = 2 \times 2^{30} = 2^{31} \quad \text{No. of Address line}$$

$$2\text{G} \times 8 = 2^{31} * 8$$

Therefore, there are 31 address lines and 8 data lines.

Total input-output lines = $31+8=39$

(iii) 16M x 32

$$1 \text{ M} = 2^{20}$$

$$16\text{M} = 2^4 \times 2^{20} = 2^{24}$$

16M x 32 can be written as

$$16\text{M} \times 32 = 2^{24} \times 32$$

No. of Address line

Therefore, there are 24 address lines and 32 data lines.

$$\text{Total input-output lines} = 24 + 32 = 56$$

(iv) 256K x 64

$$\text{Since, } 1\text{K} = 1024 = 2^{10}$$

$$256\text{K} = 2^8 \times 2^{10} = 2^{18}$$

$$256\text{K} \times 64 \text{ can be written as } 2^{18} \times 64$$

No. of Address line

Therefore, there are 18 address lines and 64 data lines.

$$\text{Total input-output lines} = 18 + 64 = 82$$

EXAMPLE 2: Give the number of bytes stored in the memories listed in example 1.

SOLUTION:

(i) 4K x 16

A byte is equivalent to 8 bits.

No. of 16 bit words = 4K = $4 * 1024 = 2^{12} = 4096$

Memory Size = No. of words * word size = $4096 * 16 \text{ bit} = 65536 \text{ bits}$

(Output is 16 i.e. 2 bytes)

Memory size = $65536 / 8 = 8192 \text{ bytes} = 8\text{kB}$

(ii) 2G x 8

A byte is equivalent to 8 bits.

No. of 8 bit words = 2G = $2G = 2 * 2^{30} = 2^{31} = 2,147,483,648$

Memory Size = No. of words * word size = $2,147,483,648 * 8 \text{ bit} = 17179869184 \text{ bits}$

(Output is 8 i.e. 1 bytes)

Memory size = $17179869184 / 8 = 2,147,483,648 = 2\text{GB}$

(iii) 16 M x 32

A byte is equivalent to 8 bits.

$$\text{No. of 16 bit words} = 2^4 \times 2^{20} = 2^{24} = 16777216$$

$$\text{Memory Size} = \text{No. of words} \times \text{word size} = 16777216 \times 32 \text{ bit} = 536870912 \text{ bits}$$

(Output is 32 i.e. 4 bytes)

$$\text{Memory size} = 536870912 / 8 = 67108864 \text{ bytes} = 64 \text{ MB}$$

Alternate 1: $16\text{M} = 2^{24}$ 

$$16 \text{ M} \times 32 = 2^{24} \times 4 \times 8 = 2^{24} \times 2^2 \times 8 = 2^{26} \times 8$$

$$\text{No. of Bytes stored} = 2^{26} = 67108864 \text{ bytes} = 64 \text{ MB}$$

Alternate 2: $\text{Memory Size} = \text{No. of words} \times \text{word size}$
 $= 16 \text{ M} \times 4 \text{ B} = 64 \text{ MB}$

(iv) 256K x 64

$$256\text{K} \times 64$$

$$\begin{aligned} \text{Memory Size} &= \text{No. of words} \times \text{word size} \\ &= 256 \text{ k} \times 8\text{B} \\ &= 2048 \text{ kB} = 2 \text{ MB} \end{aligned}$$

TYPES OF ROM

- Mask Programmed ROM (MROM)
- Programmable Read Only Memory (PROM)
- Erasable Programmable Read Only Memory (EPROM)
- E²PROM

ADVANTAGES OF ROM

- Low Cost
- High Speed
- Flexibility in system designed
- ROM is non-volatile memory.

APPLICATIONS OF ROM

- It is used for the implementation of combinational circuits.
- It is used for the implementation of sequential circuits.
- Used for look up tables.
- Used for storage purpose of microprocessor program.
- It is suitable for the LSI manufacturing process.
- Used in function generators.

INTERNAL STRUCTURE OF ROM

256 interconnections and each interconnection is programmable

 


Fig. 3

Each OR gate has 32 inputs

8 Data Output

EXAMPLE: Consider 32 x 8 ROM.

- It consists of 32 words of 8 bits each.
- To access 32 locations (addresses) there are 5 input lines ($m = 32$, $m = 2^5$, $k = 5$) which forms the binary numbers equivalent to 0 to 31.
- Fig.5 shows the internal logic of a ROM.
- The five inputs are decoded into 32 different outputs with the help of a 5 x 32 decoder and each output of the decoder represent a memory address.
- The 32 outputs of the decoder are connected to each of the eight OR gates. It means that each OR gate having 32 inputs.

- There are 8 OR gates and each OR gate has 32 connections, therefore total internal connections will be $32 \times 8 = 256$
- In general ' $2^k \times n$ ' ROM will have ' $k \times 2^k$ ' decoder and ' n ' OR gates.
- Each OR gate has 2^k inputs, which are connected to each of the outputs of the decoder.

- All 256 intersections are programmable.
- A programmable connection between two lines is equivalent to a switch which is either turned ON or OFF. ON means two lines are connected with each other and OFF means two lines are not connected.
- ROM truth table is shown in fig.4
- Truth table shows that there are 5 inputs and 8 outputs.
- There are 32 locations (addresses) and each location stored 8 bits word.
- ‘0’ in truth table indicates there is no connection and ‘1’ indicates a connection.

TRUTH TABLE:

Location No.	Inputs					Outputs							
	I ₄	I ₃	I ₂	I ₁	I ₀	A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	1	0	0	1	0	0	1	1
1	0	0	0	0	1	0	0	0	1	1	1	0	1
2	0	0	0	1	0	1	0	1	1	0	0	0	1
3	0	0	0	1	1	1	0	0	0	1	1	1	0
⋮													
⋮													
29	1	1	1	0	1	1	0	0	0	1	0	1	0
30	1	1	1	1	0	0	1	1	1	0	0	0	1
31	1	1	1	1	1	0	1	1	0	0	0	1	1

Fig. 4

INTERNAL STRUCTURE OF 32 x 8 ROM

 


Fig. 3

THANK YOU